

O módulo *Keyboard Reader* é constituído por três blocos principais: i) o decodificador de teclado (*Key Decode*); ii) o bloco de armazenamento (designado por *Ring Buffer*); e iii) o bloco de entrega ao consumidor (designado por *Output Buffer*). Neste caso o módulo *Control*, implementado em *software*, é a entidade consumidora.


 



Figura 1 – Diagrama de blocos do módulo *Keyboard Reader*
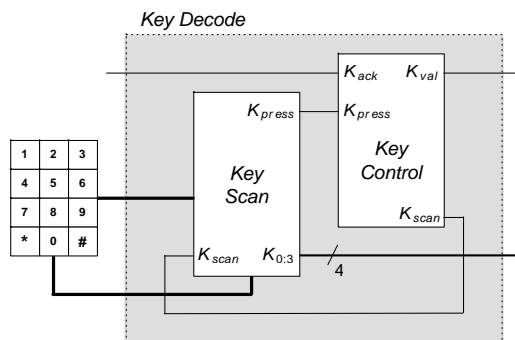
## 1 Key Decode

O bloco *Key Decode* implementa um decodificador de um teclado matricial 4x3 por *hardware*, sendo constituído por três sub-blocos: i) um teclado matricial de 4x3; ii) o bloco *Key Scan*, responsável pelo varrimento do teclado; e iii) o bloco *Key Control*, que realiza o controlo do varrimento e o controlo de fluxo, conforme o diagrama de blocos representado na Figura 2a. O controlo de fluxo de saída do bloco *Key Decode* (para o módulo *Key Buffer*), define que o sinal  $K_{val}$  é ativado quando é detetada a pressão de uma tecla, sendo também disponibilizado o código dessa tecla no barramento  $K_{0:3}$ . Apenas é iniciado um novo ciclo de varrimento ao teclado quando o sinal  $K_{ack}$  for ativado e a tecla premida for libertada. O diagrama temporal do controlo de fluxo está representado na Figura 2b.



a) Diagrama de blocos

 

b) Diagrama temporal

Figura 2 – Bloco *Key Decode*

O bloco *Key Scan* foi implementado de acordo com o diagrama de blocos representado na Figura 3. Esta versão

foi escolhida devido a ter sido a primeira versão a ser estudada, feita e testada com sucesso, pelo que para esta avaliação intercalar não faria sentido mudar. Na discussão final, iremos defender o porquê de usarmos esta versão.

O bloco *Key Control* foi implementado pela máquina de estados representada em *ASM-chart* na figura 4. Para este *ASM-chart*, a forma que ele foi concebido foi a seguinte: no primeiro estado (*STATE\_SCANNING*) este estado irá estar a fazer o varrimento do teclado, ou seja, terá de ter  $K_{scan}$  ativo (esta ativo pois tem de deixar o Contador do *Key Scan* contar) e vai estar a espera que seja premida alguma tecla do teclado ( $K_{press}$  estar ativo) para que esteja pronto para passar para o estado seguinte. No segundo estado (*STATE\_SEARCHING*) temos  $K_{val}$  ativo (ativado pois é detetada a pressão de uma tecla) e esperamos que o sinal  $K_{ack}$  seja ativo para que saibamos que a tecla que o utilizador pressionou está válida. Assim que  $K_{ack}$  estiver ativo iremos passar para o terceiro estado (*STATE\_WAITING*) em que consiste em saber qual tecla o utilizador pressionou e esperar que possamos voltar a ler mais uma tecla. Para isso iremos esperar que o  $K_{ack}$  não esteja ativo e que  $K_{press}$  também não esteja ativo, o que significa que a tecla já foi lida e que podemos voltar a ler outra.

A descrição hardware do bloco *Key Decode* em *VHDL* encontra-se no Anexo B.

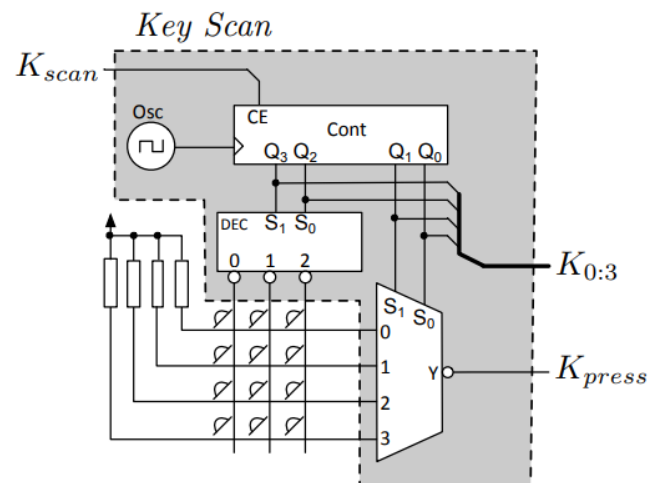


Figura 3 - Diagrama de blocos do bloco *Key Scan*

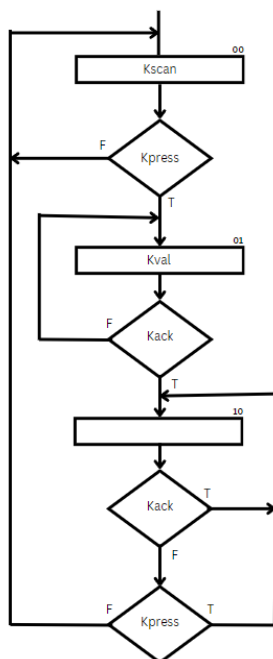


Figura 4 – Máquina de estados do bloco *Key Control*

## 2 Ring Buffer

O bloco *Ring Buffer* implementa uma estrutura de dados para armazenamento de teclas com disciplina *FIFO* (*First In First Out*), com capacidade de armazenar até oito palavras de quatro bits.

A escrita de dados no *Ring Buffer* inicia-se com a ativação do sinal DAV (*Data Available*) pelo sistema produtor, neste caso pelo *Key Decode*, indicando que tem dados para serem armazenados. Logo que tenha disponibilidade para armazenar informação, o *Ring Buffer* escreve os dados  $D_{0:3}$  em memória. Concluída a escrita em memória ativa o sinal DAC (*Data Accepted*) para informar o sistema produtor que os dados foram aceites. O sistema produtor mantém o sinal DAV ativo até que DAC seja ativado. O *Ring Buffer* só desativa DAC depois de DAV ter sido desativado.

A implementação do *Ring Buffer* é baseada numa memória RAM (*Random Access Memory*). O endereço de escrita/leitura, seleccionado por *put/get*, definido pelo bloco *Memory Address Control* (MAC) composto por dois registos, que contêm o endereço de escrita e leitura, designados por *putIndex* e *getIndex* respetivamente.

O MAC suporta assim ações de *incPut* e *incGet*, gerando informação se a estrutura de dados está cheia (*Full*) ou se está vazia (*Empty*). O bloco *Ring Buffer* procede à entrega de dados à entidade consumidora, sempre que esta indique que está disponível para receber, através do sinal *Clear To Send* (CTS). Na Figura 5 é apresentado o diagrama de blocos para a estrutura do bloco *Ring Buffer*.

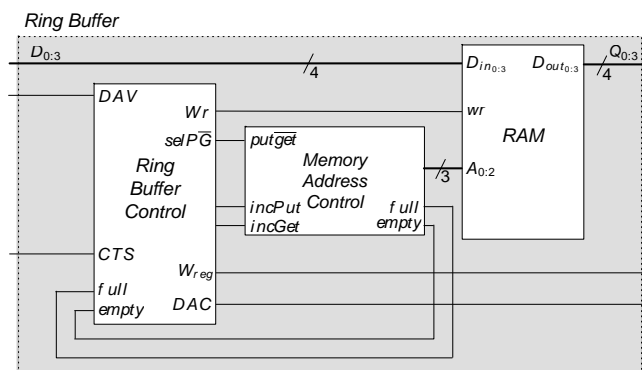


Figura 5 - Diagrama de blocos do bloco *Ring Buffer*

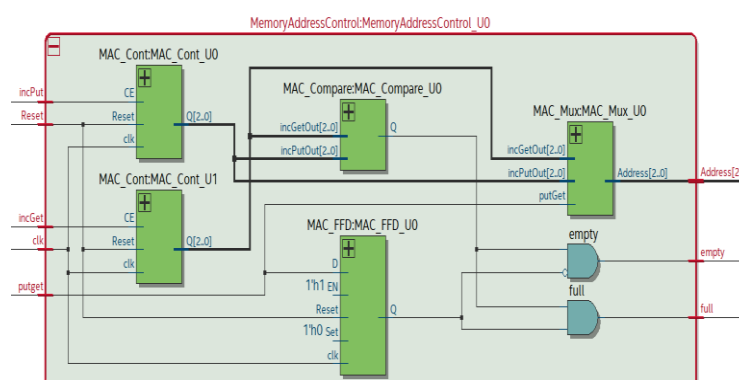


Figura 6 - Diagrama de blocos do bloco *MAC*

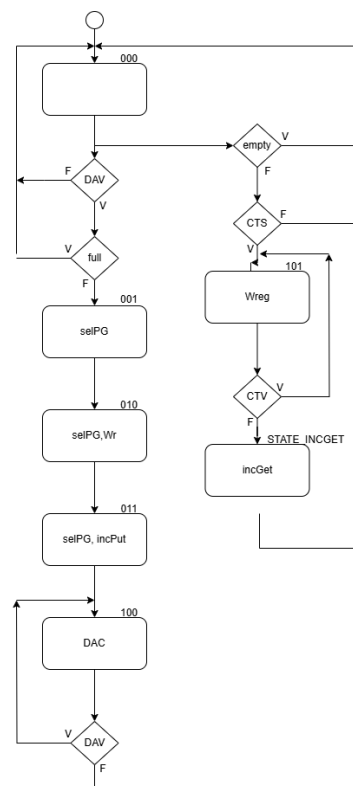


Figura 7 – Máquina de estados do bloco *Ring Buffer Control*

### 3 Output Buffer

O bloco *Output Buffer* do *Keyboard Reader* é responsável pela interação com o sistema consumidor, neste caso o módulo *Control*.

O *Output Buffer* indica que está disponível para armazenar dados através do sinal  $OB_{free}$ . Assim, nesta situação o sistema produtor pode ativar o sinal *Load* para registar os dados.

O *Control* quando pretende ler dados do *Output Buffer*, aguarda que o sinal  $D_{val}$  fique ativo, recolhe os dados e pulsa o sinal *ACK* indicando que estes já foram consumidos.

O *Output Buffer*, logo que o sinal *ACK* pulse, deve invalidar os dados baixando o sinal  $D_{val}$  e sinalizar que está novamente disponível para entregar dados ao sistema consumidor, ativando o sinal  $OB_{free}$ . Na figura 8, é apresentado o diagrama de blocos do *Output Buffer*.

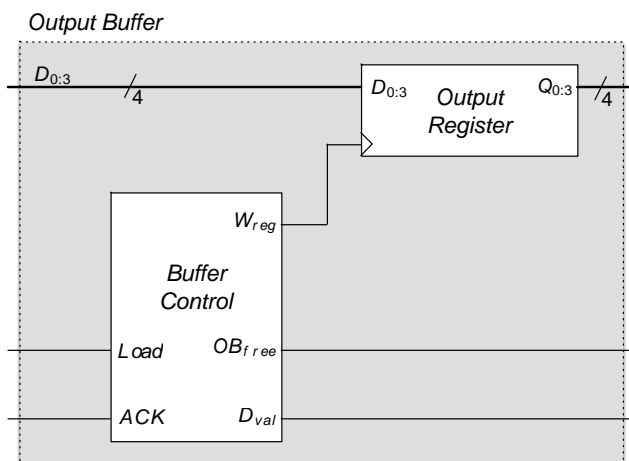


Figura 8 – Diagrama de blocos do *Output Buffer*

Sempre que o bloco emissor *Ring Buffer* tenha dados disponíveis e o bloco de entrega *Output Buffer* esteja disponível ( $OB_{free}$  ativo), o *Ring Buffer* realiza uma leitura da memória e entrega os dados ao *Output Buffer* ativando o sinal  $W_{reg}$ . O *Output Buffer* indica que já registou os dados desativando o sinal  $OB_{free}$ .

O bloco *Buffer Control* foi implementado de acordo com o ASM-chart representado na Figura 9. Para este componente, iremos ter como sinais de entrada o *Load* e o *ACK*. O *Load* tem como função indicar se temos dados para escrever e o *ACK* indica-nos se os dados já foram escritos ou não. Também teremos como saídas o  $OB_{free}$ , que indica para registar dados e  $D_{val}$ , que envia os dados para serem escritos. Esta máquina de estados tem de estar *FI* (*FullInterlock*) com a máquina do *RingBuffer Control*, para

que elas estejam interligadas entre si e para que haja sintonia.

A descrição hardware do bloco *Buffer Control* em *VHDL* encontra-se no Anexo J.

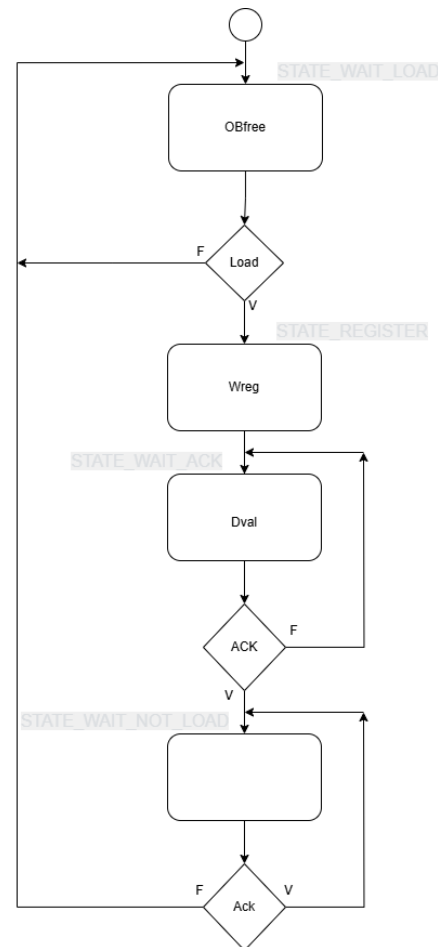


Figura 9 - Máquina de estados do bloco *Buffer Control*

Com base nas descrições do bloco *Key Decode*, *Ring Buffer* e do bloco *Key Buffer Control* implementou-se o módulo *Keyboard Reader* de acordo com o a descrição *VHDL* apresentada no Anexo A. Para este componente, tivemos de fazer a concatenação dos blocos *Key Decode*, *Ring Buffer* e *Output Buffer* e tivemos de ter em atenção cada máquina de estados para que cada uma pudesse estar *FI* (*FullInterlock*) entre si.

### 4 Interface com o *Control*

Implementou-se o módulo *Control* em *software*, recorrendo a linguagem Java e seguindo a arquitetura lógica apresentada na Figura 10.

 


Figura 10 – Diagrama lógico do módulo *Control* de interface com o módulo *Keyboard Reader*

As classes *HAL* e *KBD* desenvolvidas são descritas nas secções 4.1 e 4.2, e o código fonte desenvolvido nos Anexos L e M, respetivamente.

#### 4.1 Classe *HAL*

Este Módulo tem como objetivo escrever e ler os bits no *UsbPort* para isso desenvolvemos as seguintes funções.

*Init()* - inicia o modulo e permite começar a leitura e escrita.

*isBit(mask: Int)* - retorna true se o bit tiver o valor lógico '1'.

*readBits(mask: Int)* - lê os bits no usbport usando a máscara como "filtro".

*writeBits(mask: Int, value: Int)* - escreve no usbport o value usando a mask.

*setBits(mask: Int)* - coloca os bits do usbport a '1' de acordo com a máscara.

*clrBits(mask: Int)* - coloca os bits do usbport a '0' de acordo com a máscara.

#### 4.2 Classe *KBD*

Este Módulo tem como objetivo ler as teclas premidas na placa, para isso desenvolvemos as seguintes funções.

*init()* – limpamos o usbport para fazer a leitura dos valores.

*getKey()* – retorna a tecla premida ou none.

*waitKey(timeout: Long)* – retorna a Tecla premida se ocorrer antes do timeout(milissegundos), se não, retorna none.

## 5 Conclusões

O módulo *Keyboard Reader* é composto por três blocos principais: *Key Decode*, *Ring Buffer* e *Output Buffer*.

1. *Key Decode*: Descodifica as entradas de um teclado matricial 4x3, composto por *Key Scan* (varrimento do teclado), *Key Control* (controle do fluxo de varrimento e sinais) e o teclado matricial. Utiliza sinais como *Kval* e *Kack* para garantir a leitura correta e sincronizada das teclas.

2. *Ring Buffer*: Implementa um *buffer FIFO* que armazena até oito palavras de quatro *bits*, garantindo a ordem correta das teclas pressionadas. Comunica com o *Key Decode* através dos sinais *DAV* e *DAC* e controla a leitura e escrita usando os registos *putIndex* e *getIndex* monitorados pelo *MAC (Memory Address Control)*.

3. *Output Buffer*: Facilita a interação com o módulo *Control* em *software*, gerindo a disponibilidade e validação de dados com sinais *OBfree* e *Dval*, permitindo uma leitura eficiente das teclas pelo *Control*.

A implementação em *VHDL* assegura a interligação e sincronização dos blocos, enquanto a comunicação com o *Control* é feita via *software* em Java (kotlin). A classe *HAL* lida com a leitura e escrita na porta *USB* e a classe *KBD* facilita a leitura das teclas.

Finalizando, o módulo *Keyboard Reader* foi projetado para garantir uma leitura precisa e eficiente das teclas, armazenando-as corretamente e disponibilizando-as ao consumidor de forma sincronizada, essencial para aplicações que requerem precisão na captura de entradas de teclado.

## A. Descrição VHDL do bloco *Keyboard Reader*

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyboardReader is
port(
Line : in std_logic_vector(3 downto 0);
Reset, clk, ACK: in std_logic;
Dval : out std_logic;
Col : out std_logic_vector(2 downto 0);
Q : out std_logic_vector(3 downto 0)
);
end KeyboardReader;

architecture behavioral of KeyboardReader is

component KeyDecode is
port(
Reset: in std_logic;
clk: in std_logic;
Line: in std_logic_vector(3 downto 0);
Kack: in std_logic;
Col: out std_logic_vector(2 downto 0);
Kval: out std_logic;
K: out std_logic_vector(3 downto 0)
);
end component;

component RingBuffer is
port(
DAV, CTS, clk, Reset: in std_logic;
D: in std_logic_vector(3 downto 0);
Q: out std_logic_vector(3 downto 0);
Wreg, DAC: out std_logic
);
end component;

component OutputBuffer is
port(
D : in std_logic_vector(3 downto 0);
Load, Reset, ACK, clk: in std_logic;
Q : out std_logic_vector(3 downto 0);
OBfree, Dval : out std_logic
);
end component;

signal term0, term1, term3, term5 : std_logic;
signal term2, term4 : std_logic_vector(3 downto 0);

begin

KeyDecode_U0: KeyDecode port map(
Reset => Reset,
clk => clk,
Line => Line,
Kack => term0,
Col => Col,
Kval => term1,
K => term2
```

```
);  
  
RingBuffer_U0: RingBuffer port map(  
  DAV => term1,  
  CTS => term3,  
  clk => clk,  
  Reset => Reset,  
  D => term2,  
  Q => term4,  
  Wreg => term5,  
  DAC => term0  
);  
  
OutputBuffer_U0: OutputBuffer port map(  
  D => term4,  
  Load => term5,  
  Reset => Reset,  
  ACK => ACK,  
  clk => clk,  
  Q => Q,  
  OBfree => term3,  
  Dval => Dval  
);  
  
end behavioral;
```

## B. Descricao VHDL do bloco KeyDecode

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity KeyDecode is  
  port(  
    Reset: in std_logic;  
    CLK: in std_logic;  
    Linhas: in std_logic_vector(3 downto 0);  
    Kack: in std_logic;  
    Col: out std_logic_vector(2 downto 0);  
    Kval: out std_logic;  
    K: out std_logic_vector(3 downto 0)  
  );  
end KeyDecode;  
  
architecture behavioral of KeyDecode is  
  
  component KeyScan is  
    port(  
      Kscan: in std_logic;  
      Linhas: in std_logic_vector(3 downto 0);  
      clk: in std_logic;  
      Reset: in std_logic;  
      K: out std_logic_vector(3 downto 0);  
      Kpress: out std_logic;  
      Col: out std_logic_vector(2 downto 0)  
    );  
  end component;  
  
  component CLKdiv is  
    generic(div: natural := 50000000);  
    port ( clk_in: in std_logic;
```

```
        clk_out: out std_logic);
end component;

component KeyControl is
port(
    Reset: in std_logic;
    clk: in std_logic;
    Kack: in std_logic;
    Kpress: in std_logic;
    Kval: out std_logic;
    Kscan: out std_logic
);
end component;

signal term0, term1, not_clk, virtualclk: std_logic;

begin

not_clk <= not virtualclk;

U0 : clkDIV generic map (10000) port map(
    clk_in => clk,
    clk_out => virtualclk
);

KeyScan_Unit0: KeyScan port map(
    Kscan => term0,
    Linhas => Linhas,
    CLK => virtualCLK,
    Reset => Reset,
    K => K,
    Kpress => term1,
    Col => Col
);

KeyControl_Unit0: KeyControl port map(
    Reset => Reset,
    CLK => not_clk,
    Kack => Kack,
    Kpress => term1,
    Kval => Kval,
    Kscan => term0
);

end behavioral;
```

## C. Descrição VHDL do bloco KeyControl

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity KeyControl is
port(
    Reset: in std_logic;
    CLK: in std_logic;
    Kack: in std_logic;
    Kpress: in std_logic;
    Kval: out std_logic;
    Kscan: out std_logic
);
```

```

end KeyControl;

architecture behavioral of KeyControl is

type STATE_TYPE is (STATE_SCANNING, STATE_SEARCHING, STATE_WAITING);

signal CurrentState, NextState : STATE_TYPE;

begin

-- Flip-Flop's
CurrentState <= STATE_SCANNING when Reset = '1' else NextState when rising_edge(clk);

-- Generate Next State
GenerateNextState:
process (CurrentState, Kack, Kpress)
begin
    case CurrentState is
        when STATE_SCANNING => if (Kpress = '1') then
                                NextState <= STATE_SEARCHING;
                                else NextState <= STATE_SCANNING;
                                end if;

        when STATE_SEARCHING => if (Kack = '1') then
                                NextState <= STATE_WAITING;
                                else NextState <= STATE_SEARCHING;
                                end if;

        when STATE_WAITING => if (Kack = '0' and Kpress = '0') then
                                NextState <= STATE_SCANNING;
                                else NextState <= STATE_WAITING;
                                end if;

    end case;
end process;

-- Generate Outputs
Kscan <= '1' when (CurrentState = STATE_SCANNING) else '0';

Kval <= '1' when (CurrentState = STATE_SEARCHING) else '0';

end behavioral;

```

## D. Descrição VHDL do bloco KeyScan

```

library ieee;
use ieee.std_logic_1164.all;

entity KeyScan is
port(
    Kscan: in std_logic;
    Linhas: in std_logic_vector(3 downto 0);
    clk: in std_logic;
    Reset: in std_logic;
    K: out std_logic_vector(3 downto 0);
    Kpress: out std_logic;
    Col: out std_logic_vector(2 downto 0)
);
end KeyScan;

```



architecture behavioral of KeyScan is

component KeyScan\_Cont is

port(

CE, Reset, clk: in std\_logic;

Q: out std\_logic\_vector(3 downto 0)

);

end component;

component KeyScan\_Decoder is

port(

S: in std\_logic\_vector(1 downto 0);

Col: out std\_logic\_vector(2 downto 0)

);

end component;

component KeyScan\_Mux is

port(

Linhas: in std\_logic\_vector(3 downto 0);

S: in std\_logic\_vector(1 downto 0);

Y: out std\_logic

);

end component;

signal term: std\_logic\_vector(3 downto 0);

begin

KeyScan\_Cont\_U0: KeyScan\_Cont port map(

CE => Kscan,

Reset => Reset,

clk => clk,

Q => term

);

KeyScan\_Decoder\_U0: KeyScan\_Decoder port map(

S(0) => term(2),

S(1) => term(3),

Col => Col

);

KeyScan\_Mux\_U0: KeyScan\_Mux port map(

Linhas => Linhas,

S(0) => term(0),

S(1) => term(1),

Y => Kpress

);

K <= term;

end behavioral;

## E. Descrição VHDL do bloco Ring Buffer

library ieee;

use ieee.std\_logic\_1164.all;

entity RingBuffer is

port(

DAV, CTS, clk, Reset: in std\_logic;

D: in std\_logic\_vector(3 downto 0);

Q: out std\_logic\_vector(3 downto 0);

```

    Wreg, DAC: out std_logic
);
end RingBuffer;

architecture behavioral of RingBuffer is

component RingBufferControl port(
    Reset, clk, DAV, CTS, full, empty: in std_logic;
    Wr, selPG, Wreg, DAC, incPut, incGet: out std_logic
);
end component;

component MemoryAddressControl port(
    putget, incPut, incGet, Reset, clk: in std_logic;
    full, empty: out std_logic;
    Address: out std_logic_vector(2 downto 0)
);
end component;

component RAM
    generic(
        ADDRESS_WIDTH : natural := 3;
        DATA_WIDTH : natural := 4
    );
    port(
        address : in std_logic_vector(ADDRESS_WIDTH - 1 downto 0);
        wr: in std_logic;
        din: in std_logic_vector(DATA_WIDTH - 1 downto 0);
        dout: out std_logic_vector(DATA_WIDTH - 1 downto 0)
    );
end component;

signal term0, term1, term2, term3, term4, term5: std_logic;
signal term6: std_logic_vector(2 downto 0);
begin

RingBufferControl_U0: RingBufferControl port map(

    Reset => Reset,
    clk => clk,
    DAV => DAV,
    CTS => CTS,
    full => term0,
    empty => term1,
    Wr => term2,
    selPG => term3,
    Wreg => Wreg,
    DAC => DAC,
    incPut => term4,
    incGet => term5
);

MemoryAddressControl_U0: MemoryAddressControl port map(
    putget => term3,
    incPut => term4,
    incGet => term5,
    Reset => Reset,
    clk => clk,
    full => term0,

```

```

    empty => term1,
    Address => term6
  );

  RAM_U0: RAM port map(
    address => term6,
    wr => term2,
    din => D,
    dout => Q
  );

end behavioral;
```

## F. Descrição VHDL do bloco Ring Buffer Control

```

library ieee;
use ieee.std_logic_1164.all;

entity RingBufferControl is
  port(
    Reset, clk, DAV, CTS, full, empty: in std_logic;
    Wr, selPG, Wreg, DAC, incPut, incGet: out std_logic
  );
end RingBufferControl;

architecture behavioral of RingBufferControl is

  type STATE_TYPE is (STATE_000, STATE_001, STATE_010, STATE_011, STATE_100, STATE_101,
    STATE_INCGET);

  signal CurrentState, NextState : STATE_TYPE;

begin

  -- Flip-Flop's
  CurrentState <= STATE_000 when Reset = '1' else NextState when rising_edge(clk);

  -- Generate Next State
  GenerateNextState:
  process (CurrentState, DAV, CTS, full, empty)
  begin
    case CurrentState is
      when STATE_000 => if (DAV = '1' and full = '0') then NextState <= STATE_001;
                                                                    elsif (empty = '0' and CTS = '1') then
NextState <= STATE_101;
                                                                    else NextState <=
STATE_000;
                                                                    end if;

      when STATE_001 => NextState <= STATE_010;

      when STATE_010 => NextState <= STATE_011;

      when STATE_011 => NextState <= STATE_100;

      when STATE_100 => if (DAV = '0') then NextState <= STATE_000;
                                                                    else NextState <= STATE_100;
                                                                    end if;
    end case;
  end process;
end architecture;
```

```

when STATE_101 => if (CTS = '0') then NextState <= STATE_INCGET;
                                else NextState <= STATE_101;
                                end if;

when STATE_INCGET => NextState <= STATE_000;

end case;
end process;

Wr <= '1' when (CurrentState = STATE_010) else '0';
selPG <= '1' when (CurrentState = STATE_001 or CurrentState = STATE_010 or CurrentState = STATE_011) else '0';
Wreg <= '1' when (CurrentState = STATE_101) else '0';
DAC <= '1' when (CurrentState = STATE_100) else '0';
incPut <= '1' when (CurrentState = STATE_011) else '0';
incGet <= '1' when (CurrentState = STATE_INCGET) else '0';

end behavioral;

```

## G. Descrição VHDL do bloco Memmory Address Control

```

library ieee;
use ieee.std_logic_1164.all;

entity MemoryAddressControl is
port(
    putget, incPut, incGet, Reset, clk: in std_logic;
    full, empty: out std_logic;
    Address: out std_logic_vector(2 downto 0)
);
end MemoryAddressControl;

architecture behavioral of MemoryAddressControl is

component MAC_Cont port(
    CE, Reset, clk: in std_logic;
    Q: out std_logic_vector(2 downto 0)
);
end component;

component MAC_Mux port(
    incPutOut, incGetOut: in std_logic_vector(2 downto 0);
    putGet: in std_logic;
    Address: out std_logic_vector(2 downto 0)
);
end component;

component MAC_Compare port(
    incPutOut, incGetOut: in std_logic_vector(2 downto 0);
    Q: out std_logic
);
end component;

component MAC_FFD port(
    clk : in std_logic;
    Reset : in STD_LOGIC;
    Set : in std_logic;
    D : IN STD_LOGIC;
    EN : IN STD_LOGIC;
    Q : out std_logic
);

```

end component;

signal term0, term1: std\_logic\_vector(2 downto 0);  
signal term2, term3: std\_logic;

begin

MAC\_Cont\_U0: MAC\_Cont port map(  
    CE => incPut,  
    Reset => Reset,  
    clk => clk,  
    Q => term0  
);

MAC\_Cont\_U1: MAC\_Cont port map(  
    CE => incGet,  
    Reset => Reset,  
    clk => clk,  
    Q => term1  
);

MAC\_Mux\_U0: MAC\_Mux port map(  
    incPutOut => term0,  
    incGetOut => term1,  
    putGet => putget,  
    Address => Address  
);

MAC\_Compare\_U0: MAC\_Compare port map(  
    incPutOut => term0,  
    incGetOut => term1,  
    Q => term2  
);

MAC\_FFD\_U0: MAC\_FFD port map(  
    CLK => CLK,  
    RESET => Reset,  
    SET => '0',  
    D => putget,  
    EN => '1',  
    Q => term3  
);

full <= term2 and term3;  
empty <= term2 and not term3;

end behavioral;

## H. Descrição VHDL do bloco RAM

-----  
-- Project : DE10-Lite  
-- Affiliations: DEETC, ISEL - IPL  
-- Funding : -  
-----

-- File : RAM.vhd  
-- Author(s) : Pedro Miguens Matutino  
-- Date : 2023/01/03

-----  
-- Copyright (c) 2023 Pedro Miguens Matutino  
-----

-- Description :  
-----

-- .  
-----

library ieee;  
use ieee.std\_logic\_1164.all;  
use ieee.std\_logic\_arith.all;

entity RAM is  
generic(  
ADDRESS\_WIDTH : natural := 3;  
DATA\_WIDTH : natural := 4  
);  
port(  
address : in std\_logic\_vector(ADDRESS\_WIDTH - 1 downto 0);  
wr: in std\_logic;  
din: in std\_logic\_vector(DATA\_WIDTH - 1 downto 0);  
dout: out std\_logic\_vector(DATA\_WIDTH - 1 downto 0)  
);  
end RAM;

architecture behavioral of RAM is

type RAM\_TYPE is array (0 to 2\*\*ADDRESS\_WIDTH - 1) of std\_logic\_vector(DATA\_WIDTH - 1 downto 0);  
signal ram : RAM\_TYPE;

begin

process(address, wr)  
begin  
dout <= ram(conv\_integer(unsigned(address)));

if (wr='1') then  
ram(conv\_integer(unsigned(address))) <= din;  
end if;  
end process;

end behavioral;

## I. Descrição VHDL do bloco Output Buffer

library ieee;  
use ieee.std\_logic\_1164.all;

entity OutputBuffer is  
port(  
D : in std\_logic\_vector(3 downto 0);  
Load, Reset, ACK, clk: in std\_logic;  
Q : out std\_logic\_vector(3 downto 0);  
OBfree, Dval : out std\_logic  
);  
end OutputBuffer;

architecture behavioral of OutputBuffer is

```
component OutputRegister is
port(
D : in std_logic_vector(3 downto 0);
clk : in std_logic;
E : in std_logic;
Reset : in std_logic;
Q : out std_logic_vector(3 downto 0)
);
end component;
```

```
component BufferControl is
port(
Reset, clk, Load, ACK: in std_logic;
OBfree, Wreg, Dval: out std_logic
);
end component;
```

```
signal term0: std_logic;
```

```
begin
```

```
BufferControl_U0: BufferControl port map(
Reset => Reset,
clk => clk,
Load => Load,
ACK => ACK,
OBfree => OBfree,
Wreg => term0,
Dval => Dval
);
```

```
OutputRegister_U0: OutputRegister port map(
D => D,
clk => term0,
E => '1',
Reset => Reset,
Q => Q
);
```

```
end behavioral;
```

## J. Descrição VHDL do bloco Buffer Control

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity BufferControl is
port(
Reset, clk, Load, ACK: in std_logic;
OBfree, Wreg, Dval: out std_logic
);
end BufferControl;
```

```
architecture behavioral of BufferControl is
```

```
type STATE_TYPE is (STATE_WAIT_LOAD, STATE_REGISTER, STATE_WAIT_ACK, STATE_WAIT_NOT_LOAD);
```

```
signal CurrentState, NextState: STATE_TYPE;
```

```
begin

-- Flip-Flop's
CurrentState <= STATE_WAIT_LOAD when Reset = '1' else NextState when rising_edge(clk);

-- Generate Next State
GenerateNextState:
process (CurrentState, Load, ACK)
begin
    case CurrentState is
        when STATE_WAIT_LOAD => if(Load = '1') then NextState <= STATE_REGISTER;
                                else NextState <= STATE_WAIT_LOAD;
                                end if;

        when STATE_REGISTER => NextState <= STATE_WAIT_ACK;

        when STATE_WAIT_ACK => if(ACK = '1') then NextState <= STATE_WAIT_LOAD;
                                else NextState <= STATE_WAIT_ACK;
                                end if;

        when STATE_WAIT_NOT_LOAD => if(ACK = '0') then NextState <= STATE_WAIT_LOAD;
                                    else NextState <= STATE_WAIT_NOT_LOAD;
                                    end if;

    end case;
end process;

OBfree <= '1' when (CurrentState = STATE_WAIT_LOAD) else '0';
Dval <= '1' when (CurrentState = STATE_WAIT_ACK) else '0';
Wreg <= '1' when (CurrentState = STATE_REGISTER) else '0';

end behavioral;
```

## K. Descrição VHDL do bloco Output Register

```
library ieee;
use ieee.std_logic_1164.all;

entity OutputRegister is
port(
    D : in std_logic_vector(3 downto 0);
    clk : in std_logic;
    E : in std_logic;
    Reset : in std_logic;
    Q : out std_logic_vector(3 downto 0)
);
end OutputRegister;

architecture behavioral of OutputRegister is

    component OutputRegister_FFD port(
        clk : in std_logic;
        Reset : in std_logic;
        Set : in std_logic;
        D : in std_logic;
        EN : in std_logic;
        Q : out std_logic
    );
```



end component;

begin

```
FFD_U0: OutputRegister_FFD port map(  
  clk => clk,  
  Reset => Reset,  
  Set => '0',  
  D => D(3),  
  EN => E,  
  Q => Q(3)  
);
```

```
FFD_U1: OutputRegister_FFD port map(  
  clk => clk,  
  Reset => Reset,  
  Set => '0',  
  D => D(2),  
  EN => E,  
  Q => Q(2)  
);
```

```
FFD_U2: OutputRegister_FFD port map(  
  clk => clk,  
  Reset => Reset,  
  Set => '0',  
  D => D(1),  
  EN => E,  
  Q => Q(1)  
);
```

```
FFD_U3: OutputRegister_FFD port map(  
  clk => clk,  
  Reset => Reset,  
  Set => '0',  
  D => D(0),  
  EN => E,  
  Q => Q(0)  
);
```

end behavioral;

## L. Código Kotlin - HAL

```
object HAL { // Virtualiza o acesso ao sistema UsbPort  
  var Lastoutput = 0  
  
  // Inicia a classe  
  fun init() {  
    Lastoutput = 0  
    UsbPort.write(Lastoutput)  
  }  
  
  // Retorna true se o bit tiver o valor lógico '1'
```

```
fun isBit(mask: Int): Boolean = UsbPort.read().and(mask) != 0

// Retorna os valores dos bits representados por mask presentes no UsbPort
fun readBits(mask: Int): Int = UsbPort.read() and mask

// Escreve nos bits representados por mask o valor de value
fun writeBits(mask: Int, value: Int){

    Lastoutput = (Lastoutput and mask.inv()) or (value and mask)

    UsbPort.write(Lastoutput)
}

// Coloca os bits representados por mask no valor lógico '1'
fun setBits(mask: Int){
    Lastoutput = Lastoutput or mask
    UsbPort.write(Lastoutput)
}

// Coloca os bits representados por mask no valor lógico '0'
fun clrBits(mask: Int){
    Lastoutput = Lastoutput and mask.inv()
    UsbPort.write(Lastoutput)
}
}
```

## **M. Código Kotlin - KBD**

```
import isel.leic.utils.Time

object KBD { // Ler teclas. Métodos retornam '0'..'9', '#', '*' ou NONE.
    const val NONE = 0
    const val KVAL_MASK = 16
    const val K_DATA_MASK = 15
    const val KACK_MASK = 128

    // Inicia a classe
    fun init() {
        HAL.clrBits(KACK_MASK)
    }

    //Retorna de imediato a tecla premida ou NONE se não há tecla premida.
    fun getKey(): Char {
        val Kval = HAL.isBit(KVAL_MASK)
        if (Kval) {
            val value = HAL.readBits(K_DATA_MASK)
            val button = when (value) {
                0 -> '1'
                1 -> '4'
                2 -> '7'
                3 -> '*'

                4 -> '2'
                5 -> '5'
                6 -> '8'
                7 -> '0'
            }
        }
    }
}
```

```
        8 -> '3'
        9 -> '6'
        10 -> '9'
        11 -> '#'
        else -> NONE.toChar()
    }

    HAL.setBits(KACK_MASK) //Kack está a TRUE

    while (HAL.isBit(KVAL_MASK));

    HAL.clrBits(KACK_MASK) // Kack está a false

    return button

}
return NONE.toChar()
}

// Retorna a tecla premida, caso ocorra antes do 'timeout' (representado em milissegundos), ou
NONE caso contrário.
fun waitKey(timeout: Long): Char {
    val time = Time.getTimeInMillis() + timeout
    while(Time.getTimeInMillis() <= time) {
        val key = getKey()
        if (key != NONE.toChar())
            return key
    }
    return NONE.toChar()
}
}
```